


## Tutor Marked Assignment ELECTRICAL CIRCUITS AND ELECTRONICS

Course Code: PHE-10  
Assignment Code: PHE-10/TMA/2021  
Max. Marks: 100

**Note:** Attempt all questions. Symbols have their usual meanings. The marks for each question are indicated against it.

---

1. State, **with reasons**, whether the following statements are True or False. (2×10)
- i) Ideal current source has zero internal resistance.
  - ii) Suppressor grid in pentode is kept at anode potential.
  - iii) Bipolar junction transistor (BJT) is a voltage controlled device.
  - iv) Highest current gain is obtained in common base configuration of an amplifier.
  - v) Ripple factor of a center tapped full wave rectifier is greater than that of a bridge rectifier, which uses four diodes.
  - vi) When same voltage is applied to both the inputs of an op-amp the output voltage is infinite.
  - vii) IC LM317 is a small signal amplifier used to amplify audio frequency voltage.
  - viii) Largest decimal number represented by a 3-digit hex number is 999.
  - ix) All the logic gates can be realized using combination of only OR and NOT gates.
  - x) In a CRO sweep generator output is given to the vertical deflection plates.
2. a) Find the Thevenin equivalent for the circuit shown in Fig. 1 between terminals *a* and *b*. Calculate the current in and the voltage across the load resistance  $R_L$ . (5)

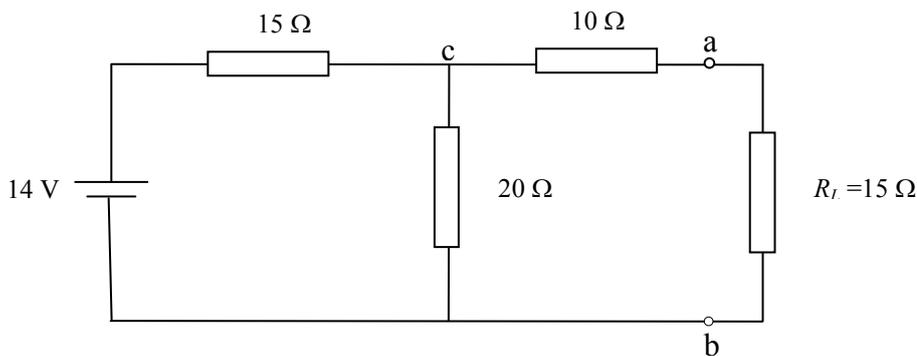

**Fig. 1**

- b) Bandwidth of an  $RLC$  series circuit is 100 kHz. If the value of  $L$  is 0.1 mH then determine the values of  $R$  and  $C$  in order to make  $Q$  of this circuit equal to 5. (5)
3. a) State the biasing conditions for  $E-B$  and  $C-B$  junctions in a BJT for its proper operation. Explain the output characteristics of a CE configuration of an amplifier. (1+4)
- b) Explain the effect of doping on the energy band diagram of a semiconductor. (5)
4. a) Why is it necessary in the case of cascade amplifier to use coupling network between the two stages? What are the advantages of transformer coupling? (2+3)

- b) On the basis of their biasing, with the help of appropriate diagrams, justify the uses of Class *A*, *AB* and *C* amplifiers for various applications. (5)
5. a) State the Barkhausen criterion for sustained oscillation. Explain the operation of Colpitts oscillator. A Colpitts oscillator oscillates with frequency 10 MHz, determine the equivalent capacitance, *C* forming tank circuit with 0.1 mH inductor. (1+2+2)
- b) The turns ratio of a transformer used in half wave rectifier is 20:1. The primary is connected to the power mains: 220 V, 50 Hz. If the diode resistance in forward bias is 20 Ω and the load resistance, *R<sub>L</sub>* is 500 Ω, determine
- the peak value, the dc value and the rms value of current;
  - the ripple factor; and
  - the rectification efficiency. (3+1+1)
6. a) You want to amplify an input signal with 10 mV amplitude and 50 MHz frequency. Which characteristics of op-amp will be significant in this case? What will be the value of these parameters? Why? (2+2+2)
- b) Design and draw a circuit using an op-amp to get + 8 V at output for input less than +4 V and -8 V at output for input greater than +4 V. (4)
7. a) For Fig. 9.4 of your study material, the formula for feedback loop gain is

$$A_{V_{cl}} = \frac{-A_V}{1 - \frac{A_V}{1 + (R_2 / R_1)}}$$

where *A<sub>V</sub>* is the fixed gain of IC380. Design and draw the circuit using IC380 to obtain the gain of 100. (5)

- b) Design a regulated power supply using LM 337 to provide -20 V output. (5)
8. a) Convert binary number 110011101<sub>2</sub> to its BCD code. (3)
- b) Divide 1010001<sub>2</sub> by 1001<sub>2</sub>. (2)
- c) Design and draw a Mod-9 counter. (5)
9. a) Design a half adder using only NAND gates. (5)
- b) Design a circuit of basic function generator to generate a triangular wave of 1 kHz frequency and ± 10 V amplitude. (5)

\*\*\*\*\*